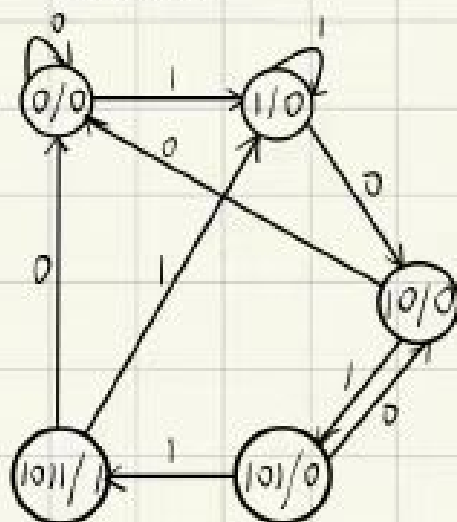


原始状态:



S_n	S_{n+1}		Z
	$x=0$	$x=1$	
0	0	1	0
1	10	1	0
10	0	101	0
101	10	1011	0
1011	0	1	1

状态分配:

$Q_2^n Q_1^n Q_0^n$	$Q_2^{n+1} Q_1^{n+1} Q_0^{n+1}$		Z
	$x=0$	$x=1$	
000	000	001	0
001	010	001	0
010	000	011	0
011	010	100	0
100	000	001	1

$$D_2 = x \bar{Q}_2 Q_1 Q_0$$

$$D_1 = \bar{x} \bar{Q}_1 \bar{Q}_0 Q_2 + \bar{x} \bar{Q}_1 Q_2 Q_0 + x \bar{Q}_2 Q_1 \bar{Q}_0$$

$$= \bar{x} \bar{Q}_1 Q_2 (\bar{Q}_0 + Q_0) + x \bar{Q}_2 Q_1 \bar{Q}_0$$


$$= \bar{x} \bar{Q}_1 Q_2 + x \bar{Q}_2 Q_1 \bar{Q}_0$$

$$D_0 = x \bar{Q}_2 Q_1 Q_0$$


$$Z = Q_2$$

001	010	001	0
010	000	011	0
011	010	100	0
100	000	001	1
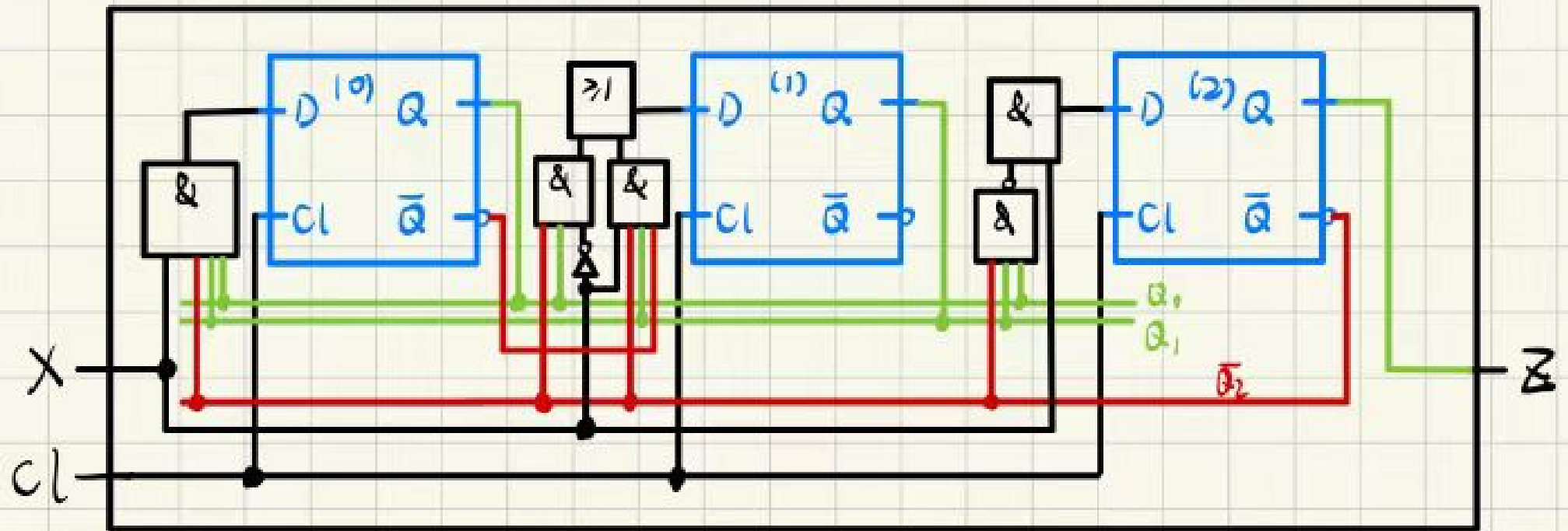
$$\begin{aligned}
 &+ X \bar{Q}_2 Q_1 Q_0 \\
 &= \bar{X} \bar{Q}_2 Q_0 + X \bar{Q}_2 Q_1 \bar{Q}_0 \\
 D_0 &= \bar{X} \bar{Q}_2 Q_0 + X \bar{Q}_2 Q_1 \bar{Q}_0 \\
 Z &= Q_2
 \end{aligned}$$



2. 原始状态:

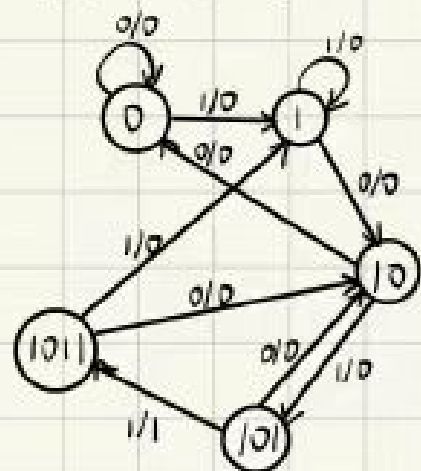

S _n	S _{n+1} / Z	
	x=0	x=1
0	0/0	1/0
1	10/0	1/0
10	0/0	101/0
101	10/0	1011/1
1011	10/0	1/0

等效

状态分配:

Q ₁ Q ₀	Q ₁ ⁿ⁺¹ Q ₀ ⁿ⁺¹ / Z / J ₁ K ₁ / J ₀ K ₀	
	x=0	x=1
00	00/0/0d/0d	01/0/0d/1d
01	10/0/1d/1d	01/0/0d/1d
10	00/0/1d/0d	11/0/1d/1d
11	10/0/0d/1d	01/1/1d/0d
01	10/0	1/0

J ₁ : Q ₁ ⁿ Q ₀ ⁿ	00	01	11	10
x	0	1	d	d
0	0	0	d	d
1	0	0	d	d

$$J_1 = \bar{Q}_1 Q_0 \bar{x}$$

K ₁ : Q ₁ ⁿ Q ₀ ⁿ	00	01	11	10
x	0	d	d	1
0	d	d	0	1
1	d	d	1	0

$$K_1 = \bar{Q}_0 \bar{x} + Q_0 x$$

J ₀ : Q ₁ ⁿ Q ₀ ⁿ	00	01	11	10
x	0	d	d	0
0	0	d	d	0
1	1	d	d	1

$$J_0 = x$$

K ₀ : Q ₁ ⁿ Q ₀ ⁿ	00	01	11	10
x	0	d	1	d
0	d	1	1	d
1	d	0	0	d

$$K_0 = \bar{x}$$

$$Z = Q_1 Q_0 x$$

01	10/0/1d/d1	01/0/0d/d0
10	00/0/d1/0d	11/0/d0/1d
11	10/0/d0/d1	01/1/d1/d0
01	10/0	1/0

x	00	01	11	10
0	d	1	1	d
1	d	0	0	d

$$Z = Q_1 Q_0 X$$

