

10. 中断异常处理对CPU设计的新要求

1) 中断异常处理数据通路升级

- ◆ 开关中断
 - 增加IE寄存器
- ◆ 保存断点
 - 增加EPC寄存器/堆栈
- ◆ 中断识别
 - 增加中断控制逻辑
- ◆ 软件支持
 - eret指令支持



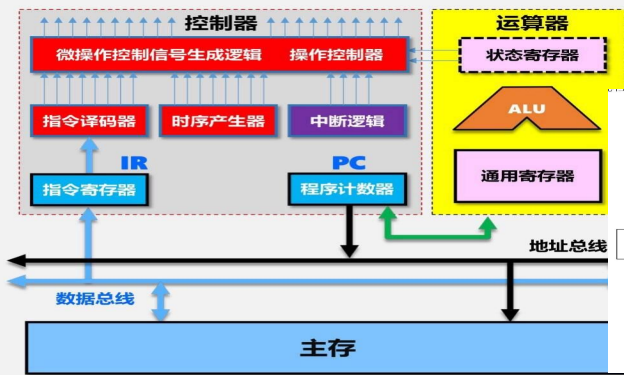
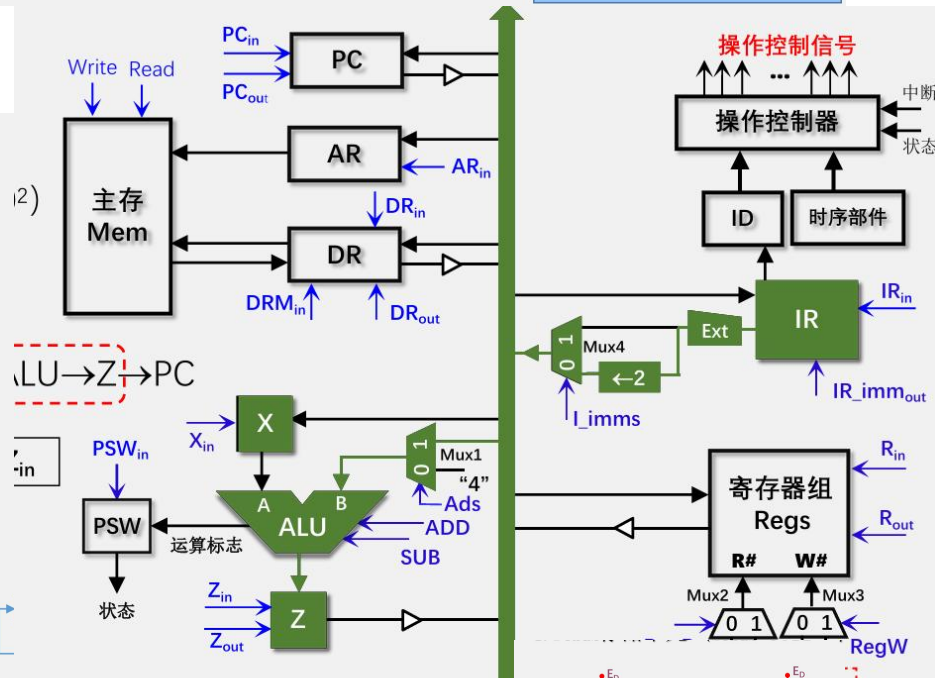
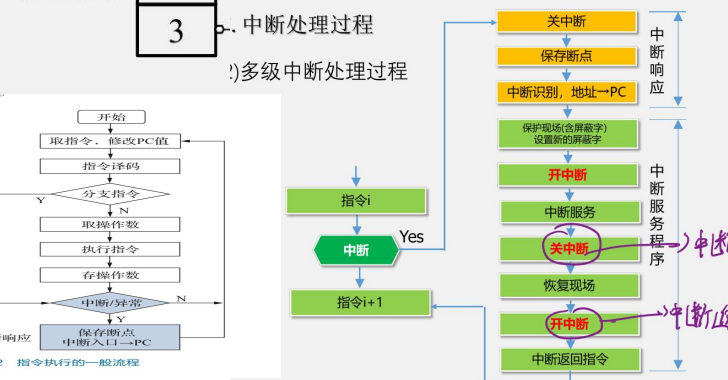
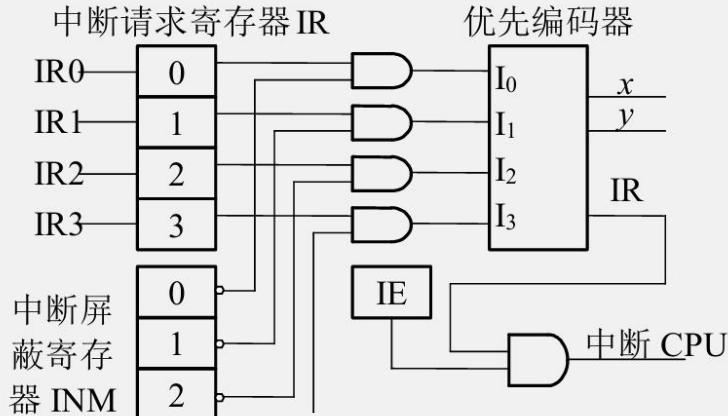
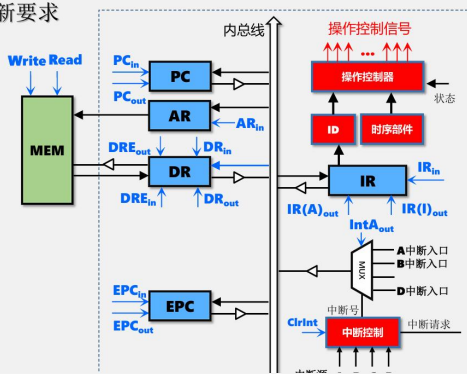



图 6.2 指令执行的一般流程

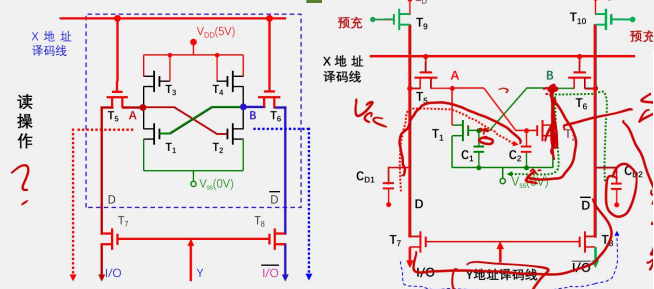


3. 字位同时扩展

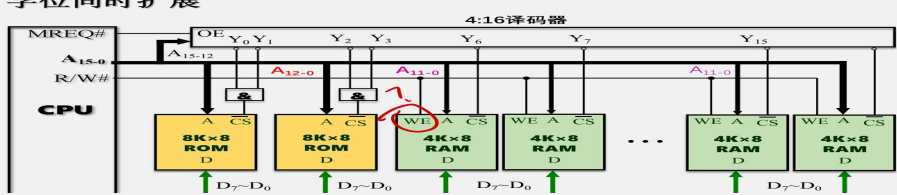

9.4 指令周期流程图

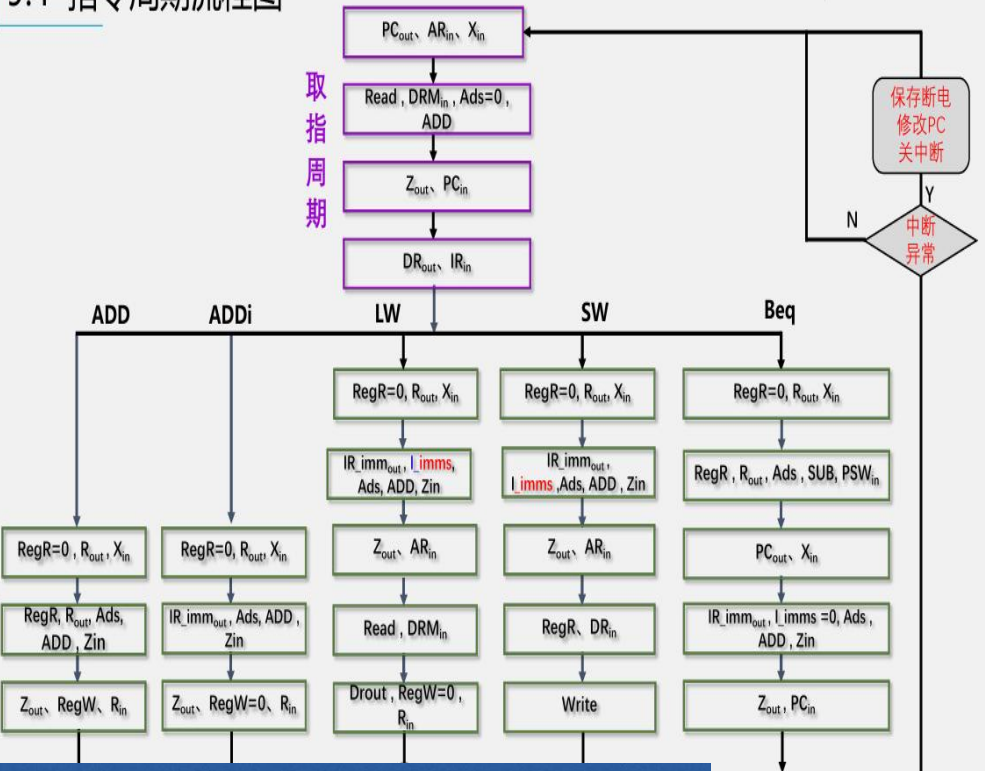



指令	PC_S(2)	RF.WE	RF.WS	RF.DS(2)	ALU_BS	DM.WE
add rd rs, rt	0 0	1	1	0 0	0	0
slt rd rs, rt	0 0	1	1	0 1	0	0
Addi rt,rs,imm	0 0	1	0	0 0	1	0
lw rt, imm(rs)	0 0	0	0	1 0	1	0
Sw rt, imm(rs)	0 0	0	0	0 0	1	1
beq rs, rt, imm*	1 0	0	0	0 0	0	0
j addr	0 1	0	0	0 0	0	0
LB rs,rt,imm	0 0	1	0	1 1	1	0

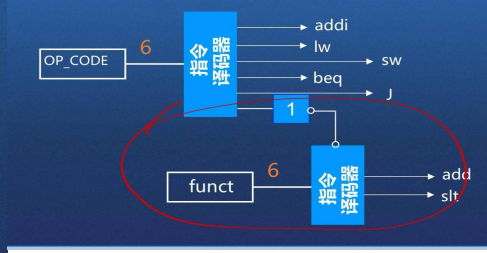

PCout、DRout、Rout、IR(A)out、Zout、IR(I)out +4、ADD、SUB writeread 填行的接口的输入指令 简化内部减低输入维

状态	微地址	操作控制字段	顺序控制字段	
0	00000			取指微程序
1	00001			
2	00010			
3	00011			
4	00100			
5	00101			
6	00110			Lw
7	00111			
8	01000			
9	01001			
10	01010			SW
11	01011			
12	01100			
13	01101			
14	01110			
15	01111			beq
16	10000			
17	10001			
18	10010			
19	10011			add
20	10100			
21	10101			
22	10110			addi
23	10111			
24	11000			

指令	PC_add	PC	PC	I[25:21]	I[20:16]	I[15:11]	ALU_Re	RF_RD1	RF_RD2	S-EXT	PCB_A	PCB_B	SL	SL2	B_EXT
add rd rs, rt	PC_add	PC	PC	I[25:21]	I[20:16]	I[15:11]	1:ALU_Re 32=1 0:ALU_Re 32=0	RF_RD1	RF_RD2						
Addi t,rs,imm	PC_add	PC	PC	I[25:21]	I[20:16]	I[15:11]		RF_RD1	S-EXT		I[15:0]				
lw rt, imm(rs)	PC_add	PC	PC	I[25:21]	I[20:16]	I[15:11]		RF_RD1	S-EXT	ALU_Re	I[15:0]				
Sw rt, imm(rs)	PCB_add	PC	PC	I[25:21]	I[20:16]	I[15:11]		RF_RD1	S-EXT	ALU_Re	I[15:0]				
j addr	SL2*	PC	PC	I[25:21]	I[20:16]	I[15:11]		RF_RD1	RF_RD2					I[25:0]	
LB rt,rs,imm	PC_add	PC	PC	I[25:21]	I[20:16]	B_EXT		RF_RD1	S-EXT		I[15:0]				DM[7:0]

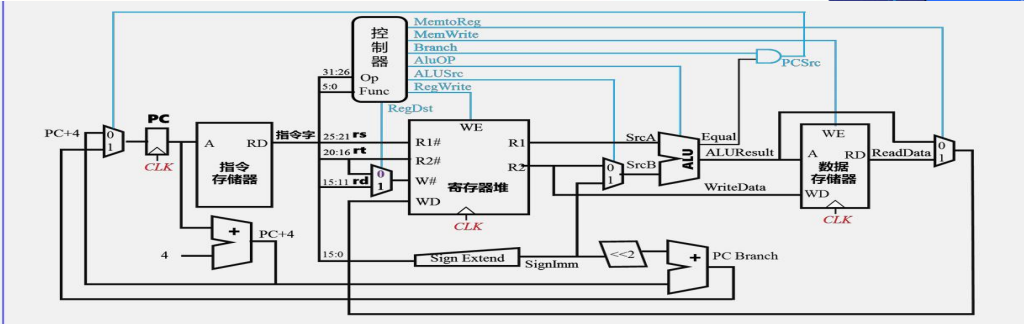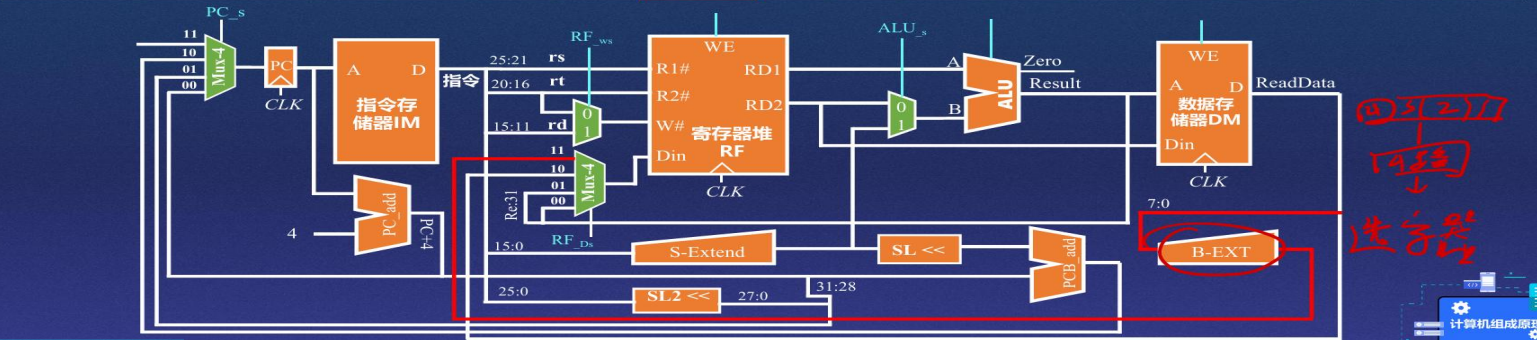

3. 字位同时扩展

